

```
-----  
--- register file implementation  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;  
  
entity regFiles is  
  
Port ( src_s0 : in std_logic;  
src_s1 : in std_logic;  
src_s2 : in std_logic;  
  
des_A0 : in std_logic;  
des_A1 : in std_logic;  
des_A2 : in std_logic;  
  
Clk : in std_logic;  
data_src : in std_logic;  
  
data : in std_logic_vector(15 downto 0);  
  
reg0 : out std_logic_vector(15 downto 0);  
reg1 : out std_logic_vector(15 downto 0);  
reg2 : out std_logic_vector(15 downto 0);  
reg3 : out std_logic_vector(15 downto 0);  
reg4 : out std_logic_vector(15 downto 0);  
reg5 : out std_logic_vector(15 downto 0);  
reg6 : out std_logic_vector(15 downto 0);  
reg7 : out std_logic_vector(15 downto 0));  
end regFiles;  
  
architecture Behavioral of regFiles is  
  
COMPONENT register4  
PORT(  
D : IN std_logic_vector(15 downto 0);  
load : IN std_logic;  
Clk : IN std_logic;  
Q : OUT std_logic_vector(15 downto 0)  
);  
  
END COMPONENT;  
  
--3 to 8 decoder.  
COMPONENT three_to_eight_decoder  
PORT(  
a0 : IN std_logic;  
a1 : IN std_logic;  
a2 : IN std_logic;  
  
q0 : OUT std_logic;  
q1 : OUT std_logic;  
q2 : OUT std_logic;  
q3 : OUT std_logic;  
q4 : OUT std_logic;  
q5 : OUT std_logic;
```

```
q6 : OUT std_logic;  
q7 : OUT std_logic  
);  
END COMPONENT;
```

--2 to 1 line MUX

```
COMPONENT mux_16bit  
PORT(  
in0 : IN std_logic_vector(15 downto 0);  
in1 : IN std_logic_vector(15 downto 0);  
s : IN std_logic;  
Z : OUT std_logic_vector(15 downto 0)  
);  
END COMPONENT;
```

--8 to 1 line multiplexer

```
COMPONENT mux8  
PORT(  
in0 : IN std_logic_vector(15 downto 0);  
in1 : IN std_logic_vector(15 downto 0);  
in2 : IN std_logic_vector(15 downto 0);  
in3 : IN std_logic_vector(15 downto 0);  
in4 : IN std_logic_vector(15 downto 0);  
in5 : IN std_logic_vector(15 downto 0);  
in6 : IN std_logic_vector(15 downto 0);  
in7 : IN std_logic_vector(15 downto 0);  
s0 : IN std_logic;  
s1 : IN std_logic;  
s2 : IN std_logic;  
Z : OUT std_logic_vector(15 downto 0)  
);  
END COMPONENT;
```

--signals

```
signal load_reg0, load_reg1, load_reg2, load_reg3 ,load_reg4  
,load_reg5 , load_reg6 , load_reg7 : std_logic;
```

```
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q,  
reg6_q, reg7_q,  
data_src_mux_out, src_reg : std_logic_vector(15 downto 0);
```

begin

--port maps for registers 0 to 7

```
-- register 0
reg00: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg0,
Clk => Clk,
Q => reg0_q
);
```

```
-- register 1
reg01: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg1,
Clk => Clk,
Q => reg1_q
);
```

```
-- register 2
reg02: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg2,
Clk => Clk,
Q => reg2_q
);
```

```
-- register 3
reg03: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg3,
Clk => Clk,
Q => reg3_q
);
```

```
-- register 4
reg04: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg4,
Clk => Clk,
Q => reg4_q
);
```

```
-- register 5
reg05: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg5,
Clk => Clk,
Q => reg5_q
);
```

```
-- register 6
reg06: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg6,
Clk => Clk,
Q => reg6_q
);
```

```
-- register 7
reg07: register4 PORT MAP(
D => data_src_mux_out,
load => load_reg7,
Clk => Clk,
Q => reg7_q
);

--destination register decoder

des_decoder_3to8: three_to_eight_decoder PORT MAP(

a0 => des_A0,
a1 => des_A1,
a2 => des_A2,

q0 => load_reg0,
q1 => load_reg1,
q2 => load_reg2,
q3 => load_reg3,
q4 => load_reg4,
q5 => load_reg5,
q6 => load_reg6,
q7 => load_reg7

);

-- 2 to 1 data source multiplexer
data_src_mux2_4bit: mux_16bit PORT MAP(
in0 => data,
in1 => src_reg,
s => data_src,
Z => data_src_mux_out
);

-- 4 to 1 source register multiplexer
Inst_mux4_4bit: mux8 PORT MAP(
in0 => reg0_q,
in1 => reg1_q,
in2 => reg2_q,
in3 => reg3_q,
in4 => reg4_q,
in5 => reg5_q,
in6 => reg6_q,
in7 => reg7_q,

s0 => src_s0,
s1 => src_s1,
s2 => src_s2,
Z => src_reg
);

reg0 <= reg0_q;
reg1 <= reg1_q;
reg2 <= reg2_q;
```

```
reg3 <= reg3_q;  
reg4 <= reg4_q;  
reg5 <= reg5_q;  
reg6 <= reg6_q;  
reg7 <= reg7_q;
```

```
end Behavioral;
```

```
-----  
-- register-16 bits  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity register4 is  
port ( D : in std_logic_vector(15 downto 0);  
load, Clk : in std_logic;  
Q : out std_logic_vector(15 downto 0));  
end register4;
```

```
architecture Behavioral of register4 is  
begin  
process (Clk)  
begin  
if (rising_edge(Clk)) then  
if load='1' then  
Q<=D after 5 ns;  
end if;  
end if;  
end process;  
end Behavioral;
```

```
-----  
-- 3 to 8 decoder 16 bits implementation  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity three_to_eight_decoder is  
port(  
a0: in std_logic;  
a1: in std_logic;  
a2: in std_logic;  
q0: out std_logic;  
q1: out std_logic;  
q2: out std_logic;  
q3: out std_logic;  
q4: out std_logic;  
q5: out std_logic;  
q6: out std_logic;  
q7: out std_logic  
);
```

```
end three_to_eight_decoder;
```

```

architecture behvOfDecoder of three_to_eight_decoder is
begin
q0<= not a0 and not a1 and not a2;
q1<= not a0 and not a1 and a2;
q2<= not a0 and a1 and not a2;
q3<= not a0 and a1 and a2;
q4<= a0 and not a1 and not a2;
q5<= a0 and not a1 and a2;
q6<= a0 and a1 and not a2;
q7<= a0 and a1 and a2;

end behvOfDecoder;

```

```

-----
--mux 2 to 1 (16 bits) implementation
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux_16bit is
port ( in0 : in std_logic_vector(15 downto 0);
in1 : in std_logic_vector(15 downto 0);
s : in std_logic;
Z : out std_logic_vector(15 downto 0));
end mux_16bit;
architecture Behavioral of mux_16bit is
begin
Z <= in0 after 5 ns when s='0' else
in1 after 5 ns when s='1'else
"0000000000000000" after 5 ns;
end Behavioral;

```

```

-----
-- mux 8 to 1 (16 bits) implementation
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux8 is
Port (
in0, in1, in2, in3, in4, in5, in6, in7: in std_logic_vector (15 downto 0);
s0, s1 ,s2: in std_logic;

Z: out std_logic_vector (15 downto 0));
end mux8;

```

```

architecture behavioural of mux8 is
begin
Z <=
in0 after 5ns when s0 = '0' and s1 = '0' and s2 = '0' else
in1 after 5ns when s0 = '0' and s1 = '0' and s2 = '1' else
in2 after 5ns when s0 = '0' and s1 = '1' and s2 = '0' else
in3 after 5ns when s0 = '0' and s1 = '1' and s2 = '1' else
in4 after 5ns when s0 = '1' and s1 = '0' and s2 = '0' else
in5 after 5ns when s0 = '1' and s1 = '0' and s2 = '1' else
in6 after 5ns when s0 = '1' and s1 = '1' and s2 = '0' else
in7 after 5ns when s0 = '1' and s1 = '1' and s2 = '1' else
X"0000" after 5ns;
end behavioural;

```

```
-----
--3 to 8 decoder test-bench
-----
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY decoder3to8_tb IS
END decoder3to8_tb;

ARCHITECTURE behavior OF decoder3to8_tb IS

```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```

COMPONENT three_to_eight_decoder
PORT (
    a0 : IN  std_logic;
    a1 : IN  std_logic;
    a2 : IN  std_logic;
    q0 : OUT std_logic;
    q1 : OUT std_logic;
    q2 : OUT std_logic;
    q3 : OUT std_logic;
    q4 : OUT std_logic;
    q5 : OUT std_logic;
    q6 : OUT std_logic;
    q7 : OUT std_logic
);
END COMPONENT;

```

```
--Inputs
```

```

signal a0 : std_logic := '0';
signal a1 : std_logic := '0';
signal a2 : std_logic := '0';

```

```
--Outputs
```

```

signal q0 : std_logic;
signal q1 : std_logic;
signal q2 : std_logic;
signal q3 : std_logic;
signal q4 : std_logic;
signal q5 : std_logic;
signal q6 : std_logic;
signal q7 : std_logic;

```

```
constant clk_period : time := 10 ns;
```

```
BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: three_to_eight_decoder PORT MAP (
    a0 => a0,
    a1 => a1,
    a2 => a2,
    q0 => q0,
    q1 => q1,
    q2 => q2,
    q3 => q3,
    q4 => q4,
    q5 => q5,
    q6 => q6,
    q7 => q7
  );

  -- Stimulus process
  stim_proc: process

  begin

    --test enable for reg 0
    wait for 10 ns;
    a0<='0';
    a1<='0';
    a2<='0';

    --test enable for reg 1
    wait for 10 ns;
    a0<='0';
    a1<='0';
    a2<='1';

    --test enable for reg 2
    wait for 10 ns;
    a0<='0';
    a1<='1';
    a2<='0';

    --test enable for reg 3
    wait for 10 ns;
    a0<='0';
    a1<='1';
    a2<='1';

    --test enable for reg 4
    wait for 10 ns;
    a0<='1';
    a1<='0';
    a2<='0';
```



```

--test enable for reg 5
wait for 10 ns;
a0<='1';
a1<='0';
a2<='1';

--test enable for reg 6
wait for 10 ns;
a0<='1';
a1<='1';
a2<='0';

--test enable for reg 7
wait for 10 ns;
a0<='1';
a1<='1';
a2<='1';

-- wait;
end process;

END;

-----
-- mux 2 to 1 (16 bits) test-bench
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux2to1_Tb IS
END mux2to1_Tb;

ARCHITECTURE behavior OF mux2to1_Tb IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT mux_16bit
PORT (
    in0 : IN  std_logic_vector(15 downto 0);
    in1 : IN  std_logic_vector(15 downto 0);
    s   : IN  std_logic;
    Z   : OUT std_logic_vector(15 downto 0)
);
END COMPONENT;

--Inputs
signal in0 : std_logic_vector(15 downto 0) := (others => '0');
signal in1 : std_logic_vector(15 downto 0) := (others => '0');
signal s   : std_logic := '0';

--Outputs
signal Z : std_logic_vector(15 downto 0);

```

```

BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: mux_16bit PORT MAP (
    in0 => in0,
    in1 => in1,
    s => s,
    z => z
  );

  -- Stimulus process
  stim_proc: process
  begin
    in0<=X"1c2d";
    in1<=X"ffff";

    wait for 100 ns;
----select input 0 -----
    s<='0';

    wait for 100 ns;
----select input 1 -----
    s<='1';
  end process;

END;

-----
-- mux 8 to 1 (16 bits) test-bench
-----

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux_tb IS
END mux_tb;

ARCHITECTURE behavior OF mux_tb IS

  -- Component Declaration for the Unit Under Test (UUT)

  COMPONENT mux8
  PORT (
    in0 : IN  std_logic_vector(15 downto 0);
    in1 : IN  std_logic_vector(15 downto 0);
    in2 : IN  std_logic_vector(15 downto 0);
    in3 : IN  std_logic_vector(15 downto 0);
    in4 : IN  std_logic_vector(15 downto 0);
    in5 : IN  std_logic_vector(15 downto 0);
    in6 : IN  std_logic_vector(15 downto 0);
    in7 : IN  std_logic_vector(15 downto 0);

```

```

    s0 : IN  std_logic;
    s1 : IN  std_logic;
    s2 : IN  std_logic;
    Z  : OUT  std_logic_vector(15 downto 0)
  );
END COMPONENT;

--Inputs
signal in0 : std_logic_vector(15 downto 0) := (others => '0');
signal in1 : std_logic_vector(15 downto 0) := (others => '0');
signal in2 : std_logic_vector(15 downto 0) := (others => '0');
signal in3 : std_logic_vector(15 downto 0) := (others => '0');
signal in4 : std_logic_vector(15 downto 0) := (others => '0');
signal in5 : std_logic_vector(15 downto 0) := (others => '0');
signal in6 : std_logic_vector(15 downto 0) := (others => '0');
signal in7 : std_logic_vector(15 downto 0) := (others => '0');
signal s0  : std_logic := '0';
signal s1  : std_logic := '0';
signal s2  : std_logic := '0';

--Outputs
signal Z : std_logic_vector(15 downto 0);

BEGIN

  -- Instantiate the Unit Under Test (UUT)
  uut: mux8 PORT MAP (
    in0 => in0,
    in1 => in1,
    in2 => in2,
    in3 => in3,
    in4 => in4,
    in5 => in5,
    in6 => in6,
    in7 => in7,
    s0 => s0,
    s1 => s1,
    s2 => s2,
    Z  => Z
  );

  -- Stimulus process
  stim_proc: process
  begin

    in0<="1111111111111111";
    in1<="1000110111111001";
    in2<="0110110111111010";
    in3<="0110010111111010";
    in4<="0110110111111010";
    in5<="0110110011111010";
    in6<="0110110110111010";
    in7<="0110110111110010";

```

```
-----in0 selected-----
    wait for 50 ns;
    s0<='0';
    s1<='0';
    s2<='0';

-----in1 selected-----

    wait for 50 ns;
    s0<='0';
    s1<='0';
    s2<='1';

-----in2 selected-----

    wait for 50 ns;
    s0<='0';
    s1<='1';
    s2<='0';

-----in3 selected-----
    wait for 50 ns;
    s0<='0';
    s1<='1';
    s2<='1';

-----in4 selected-----
    wait for 50 ns;
    s0<='1';
    s1<='0';
    s2<='0';

-----in5 selected-----
    wait for 50 ns;
    s0<='1';
    s1<='0';
    s2<='1';

-----in6 selected-----

    wait for 50 ns;
    s0<='1';
    s1<='1';
    s2<='0';

-----in7 selected-----

    wait for 50 ns;
    s0<='1';
    s1<='1';
    s2<='1';

    end process;

END;
```

```
-----  
-- register files (8 registers-16 bits) test-bench  
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY regFiles_tb IS  
END regFiles_tb;  
  
ARCHITECTURE behavior OF regFiles_tb IS  
  
    -- Component Declaration for the Unit Under Test (UUT)  
  
    COMPONENT regFiles  
    PORT (  
        src_s0 : IN  std_logic;  
        src_s1 : IN  std_logic;  
        src_s2 : IN  std_logic;  
        des_A0 : IN  std_logic;  
        des_A1 : IN  std_logic;  
        des_A2 : IN  std_logic;  
        Clk    : IN  std_logic;  
        data_src : IN  std_logic;  
        data   : IN  std_logic_vector(15 downto 0);  
        reg0   : OUT std_logic_vector(15 downto 0);  
        reg1   : OUT std_logic_vector(15 downto 0);  
        reg2   : OUT std_logic_vector(15 downto 0);  
        reg3   : OUT std_logic_vector(15 downto 0);  
        reg4   : OUT std_logic_vector(15 downto 0);  
        reg5   : OUT std_logic_vector(15 downto 0);  
        reg6   : OUT std_logic_vector(15 downto 0);  
        reg7   : OUT std_logic_vector(15 downto 0)  
    );  
    END COMPONENT;  
  
    --Inputs  
    signal src_s0 : std_logic := '0';  
    signal src_s1 : std_logic := '0';  
    signal src_s2 : std_logic := '0';  
    signal des_A0 : std_logic := '0';  
    signal des_A1 : std_logic := '0';  
    signal des_A2 : std_logic := '0';  
    signal Clk    : std_logic := '0';  
    signal data_src : std_logic := '0';  
    signal data   : std_logic_vector(15 downto 0) := (others => '0');  
  
    --Outputs  
    signal reg0 : std_logic_vector(15 downto 0);  
    signal reg1 : std_logic_vector(15 downto 0);  
    signal reg2 : std_logic_vector(15 downto 0);  
    signal reg3 : std_logic_vector(15 downto 0);  
    signal reg4 : std_logic_vector(15 downto 0);  
    signal reg5 : std_logic_vector(15 downto 0);  
    signal reg6 : std_logic_vector(15 downto 0);  
    signal reg7 : std_logic_vector(15 downto 0);
```

```

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: regFiles PORT MAP (
        src_s0 => src_s0,
        src_s1 => src_s1,
        src_s2 => src_s2,
        des_A0 => des_A0,
        des_A1 => des_A1,
        des_A2 => des_A2,
        Clk => Clk,
        data_src => data_src,
        data => data,
        reg0 => reg0,
        reg1 => reg1,
        reg2 => reg2,
        reg3 => reg3,
        reg4 => reg4,
        reg5 => reg5,
        reg6 => reg6,
        reg7 => reg7
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin

        --load arbitrary hex values into registers.
        --load hex value 3f3f to register 0
        data<=X"3f3f";
        des_A0<='0';
        des_A1<='0';
        des_A2<='0';
        data_src<='0';

        wait for 30 ns;
        --load hex value 1e5c to register 1
        data<=X"1e5c";
        des_A0<='0';
        des_A1<='0';
        des_A2<='1';
        data_src<='0';
    end process;

```

```
wait for 30 ns;  
--load hex value 2d2d to register 2  
data<=X"2d2d";  
des_A0<='0';  
des_A1<='1';  
des_A2<='0';  
data_src<='0';
```

```
wait for 30 ns;  
--load hex value 5a5a to register 3  
data<=X"5a5a";  
des_A0<='0';  
des_A1<='1';  
des_A2<='1';  
data_src<='0';
```

```
wait for 30 ns;  
--load hex value 1c2c to register 4  
data<=X"1c2c";  
des_A0<='1';  
des_A1<='0';  
des_A2<='0';  
data_src<='0';
```

```
wait for 30 ns;  
--load hex value 5B5B to register 5  
data<=X"5b5b";  
des_A0<='1';  
des_A1<='0';  
des_A2<='1';  
data_src<='0';
```

```
wait for 30 ns;  
--load hex value 7d7d to register 6  
data<=X"7d7d";  
des_A0<='1';  
des_A1<='1';  
des_A2<='0';  
data_src<='0';
```

```
wait for 30 ns;  
--load hex value ffff to register 7  
data<=X"ffff";  
des_A0<='1';  
des_A1<='1';  
des_A2<='1';  
data_src<='0';
```

```
-Transferring data from register 0 to register 1-----  
  
wait for 30 ns;  
----- selecting register 0 as source register-----  
src_s0<='0';  
src_s1<='0';  
src_s2<='0';  
  
----- selecting register 1 as destination register-----  
  
des_A0<='0';  
des_A1<='0';  
des_A2<='1';  
  
----- select input to 1 to enable transfer data(with select  
line =0 you can load your own data)-----  
data_src<='1';  
  
-----Transferring data from register 3 to register 7-----  
  
----- selecting register 3 as source register-----  
  
wait for 100 ns;  
src_s0<='0';  
src_s1<='1';  
src_s2<='1';  
  
----- selecting register 7 as destination register-----  
  
des_A0<='1';  
des_A1<='1';  
des_A2<='1';  
  
data_src<='1';  
  
wait;  
end process;  
  
END;
```



```
-----  
--single register 16 bits test-bench  
-----  
  
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY register_tb IS  
END register_tb;  
  
ARCHITECTURE behavior OF register_tb IS  
  
    -- Component Declaration for the Unit Under Test (UUT)  
  
    COMPONENT register4  
    PORT(  
        D : IN  std_logic_vector(15 downto 0);  
        load : IN  std_logic;  
        Clk : IN  std_logic;  
        Q : OUT std_logic_vector(15 downto 0)  
    );  
    END COMPONENT;  
  
    --Inputs  
    signal D : std_logic_vector(15 downto 0) := (others => '0');  
    signal load : std_logic := '0';  
    signal Clk : std_logic := '0';  
  
    --Outputs  
    signal Q : std_logic_vector(15 downto 0);  
  
    -- Clock period definitions  
    constant Clk_period : time := 10 ns;  
  
BEGIN  
  
    -- Instantiate the Unit Under Test (UUT)  
    uut: register4 PORT MAP (  
        D => D,  
        load => load,  
        Clk => Clk,  
        Q => Q  
    );  
  
    -- Clock process definitions  
    Clk_process :process  
    begin  
        Clk <= '0';  
        wait for Clk_period/2;  
        Clk <= '1';  
        wait for Clk_period/2;  
    end process;
```

```
-- Stimulus process
stim_proc: process
begin

----data wont be transfered to register as load enable bit is set to zero
    D<="1111111111111111";
    wait for 100 ns;
    load<='0';

----- loading 0111111111111111 into register when load enable = 1-----
-----
    wait for 100 ns;
    load<='1';


----- load another value into register-----
-----
    wait for 100 ns;
    D<="0000000000000000";
    wait;

end process;

END;
```

Register file test-bench simulation


Initially all registers are undefined. Arbitrary hex values are loaded into each register 0 to 7. To test the correct transfer of any register to any other register, data of register 0 is transferred to register 1 and data of register 3 is transferred to register 7. It is evident from the image below after around 250 ns contents of register 1 has changed and is identical to contents in register 0. At around 350 ns contents of register 7 are identical to contents of register 3.

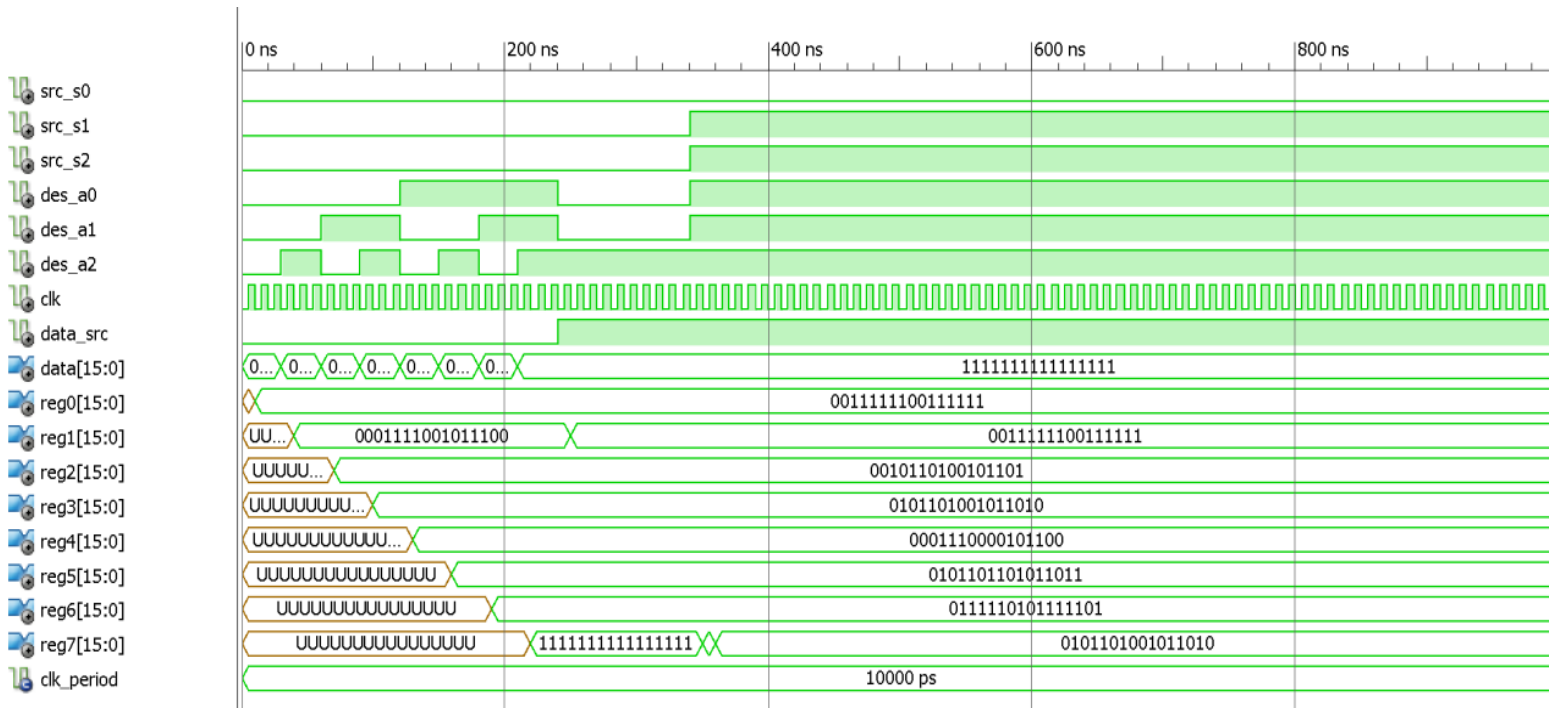

Simulation Results


Decoder 3 to 8

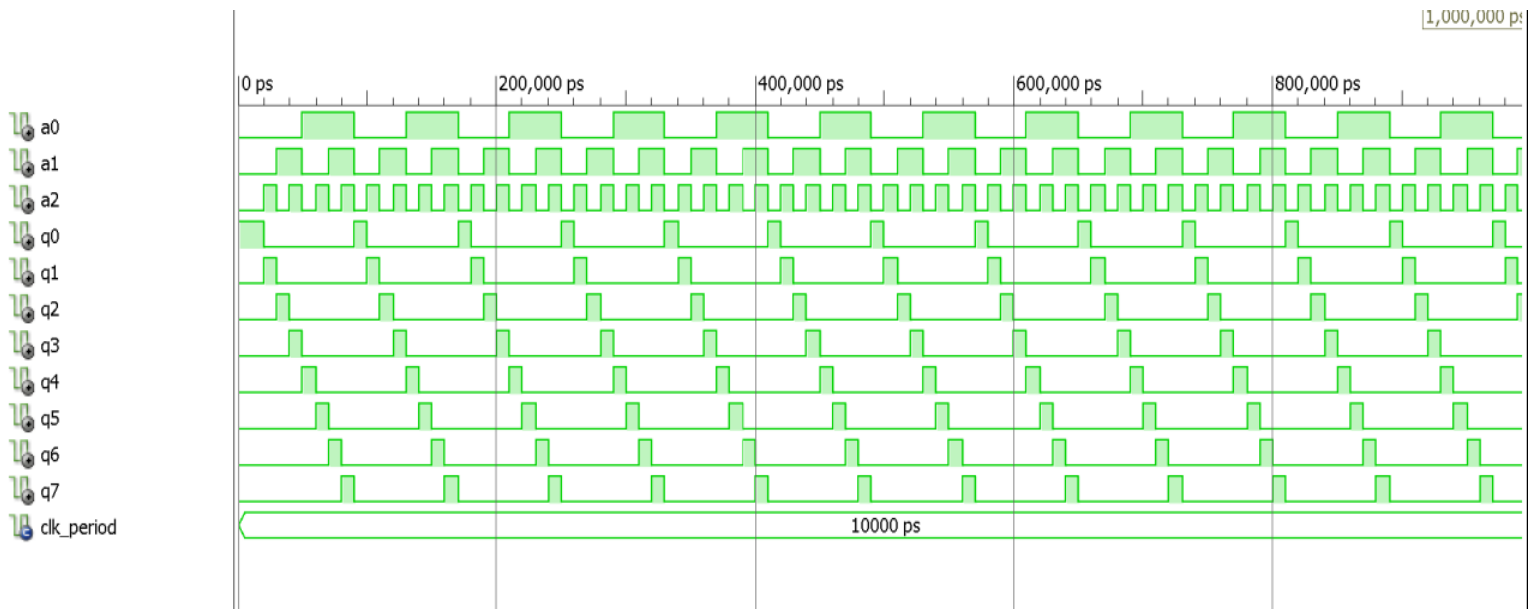When a0,a1,a2 are all low, q0 is selected. When a0,a1,a2 are all high then q7 is selected.




Mux 2 to 1 – 16 bits

 
The output, z alternates between the data in in0 and in1 as the select bit, s alternates after a fixed period of time.



Mux 8 to 1 -16 bits

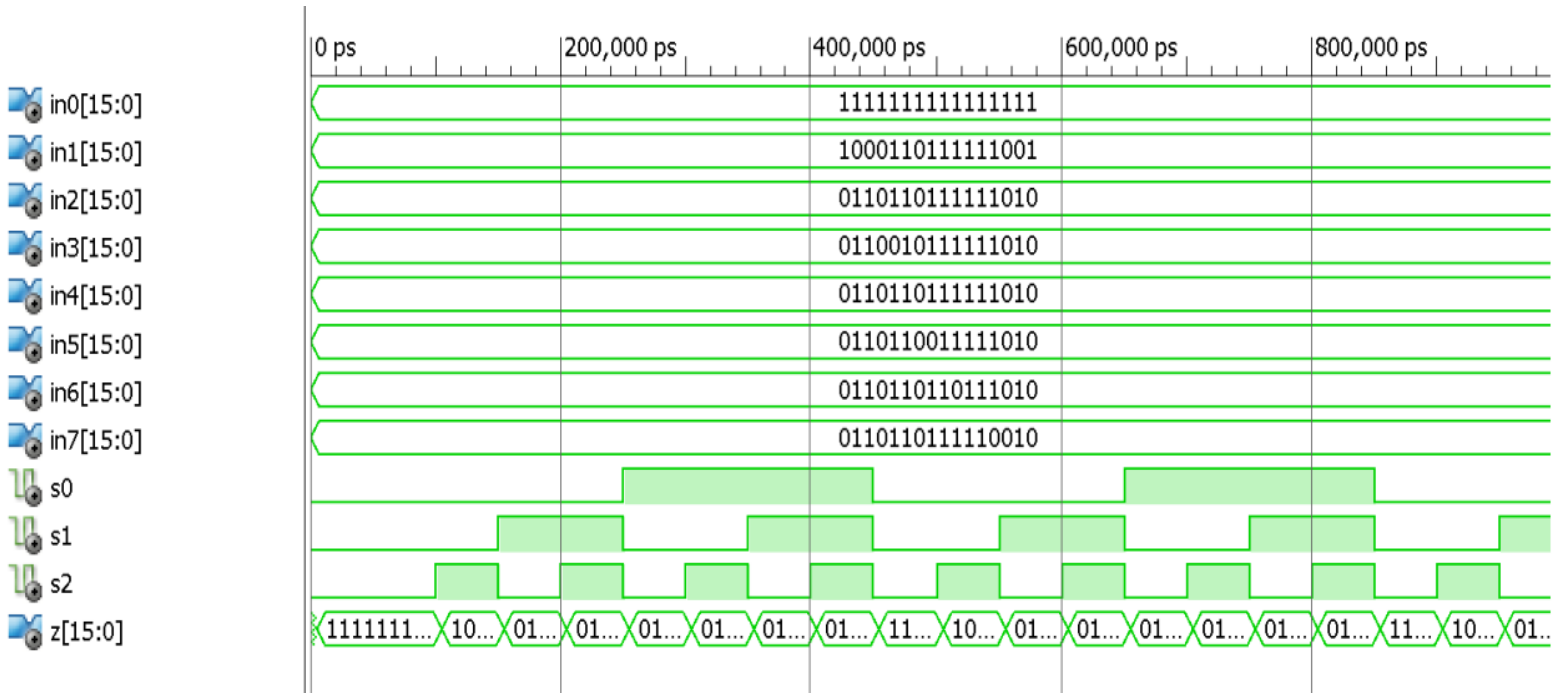

 When the select line is 010, in2 contents become the output,z.



Register- 16 bit

To test that each register works properly, at around 200 ns content of the register changes from undefined to 1111111111111111 after 100 ns contents change to 0000000000000000.

